

NAME:

NUMBER:

DATE: 24.01.2022

Q1:

Design a folded cascade OTA with pMOS transistors at the input and single ended output. The load of the OTA is 2pF. Ensure that the rising and falling Slew-rate are at least 50V/us, the GBW should be at least 50MHz and the low frequency gain should be at least 60dB. Draw the bode-plot of your designed OTA.

- Also calculate the non-dominant pole and pole-zero doublet
- Draw the bode-plot of your designed OTA.
- What is the phase margin of your OTA for unity feedback?

NAME:

NUMBER:

DATE: 24.01.2022


Q2:

For the circuit below: derive the expression for gain, bandwidth, GBW, SR and non-dominant pole.

Also calculate these values for:

$V_{DD}=3.3V$, $I_{B1}=50\mu A$, $I_{B2}=20\mu A$, $C_L=1pF$,

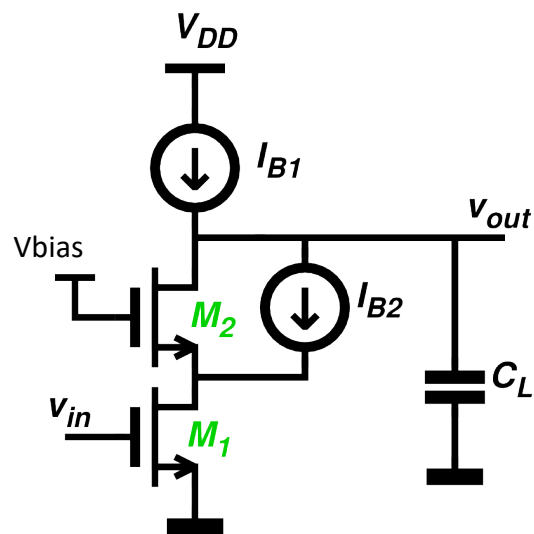$W_1=3\mu m$, $L_1=1\mu m$, $W_2=3\mu m$, $L_2=1\mu m$




NAME:

NUMBER:

DATE: 24.01.2022

Q3

 1. Amplifier A has a DC input and output voltage of 0.5 V. Derive its IM_2 for a sinusoidal input signal of 40 mV_{ptp} assuming a linear load resistor R_L .
2. Derive IM_2 of amplifier for the same conditions and the same input signal.
3. In reality, the Early voltage (V_E) is not infinity. Qualitatively discuss the effect of a realistic Early voltage on IM_2 .



$$I_{DS,n} = K'_n \frac{W}{L} (V_{GS} - V_T)^2 \left(1 + \frac{V_{DS}}{V_E L} \right)$$
$$I_{SD,p} = K'_p \frac{W}{L} (V_{SG} - V_T)^2 \left(1 + \frac{V_{SD}}{V_E L} \right)$$

V_{DD}	1 V
T	300 K
L_{min}	65 nm
K'_n	440 $\mu A/V^2$
K'_p	140 $\mu A/V^2$
V_T	0.3 V
C_{ox}	12 fF/ μm^2
V_E	∞ V/ μm